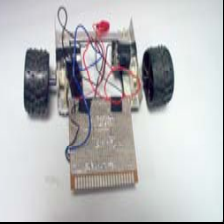


Line Following Robot

Adarsh K (ME00362)

Prashanth S (ME00370)

Radha Malini M G (ME00371)



Navigation Principles

✿ Externally Guided

✿ Laser

- ✿ Similar to the principle of Laser guided missiles.

✿ GPS Based

- ✿ Most modern method in Exploratory robots.
- ✿ Can estimate its own location within meters


✿ Self Guided

✿ CCD Camera

- ✿ Can detect using machine vision.
- ✿ Uses contrast to detect edges.

✿ Proximity Sensor



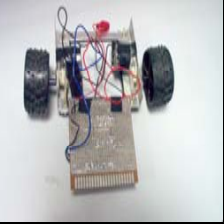

Navigation Principles

✿ Collision Avoidance

- **Combination of sensors and path finding Techniques.**
- **Can be**
 - Preprogrammed – Static.
 - Adaptive – Dynamic.

✿ Line Following

- **Used in manufacturing .**
 - Delivering parts between stations.
- **Possible to use different colored lines.**


✿ Microprocessor Controlled

- **Can be programmed to handle different conditions.**

✿ Electronic Controlled

- **Hard Wired.**
- **Cheap and simple.**
- **Manual switching for handling different conditions.**


Line Following Robots

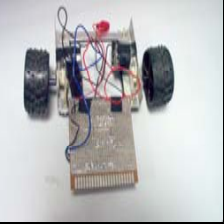

Sandwich





Sweet

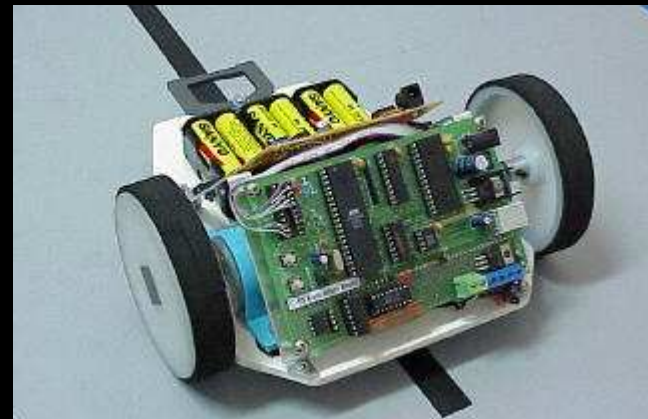

Kabo


Line Following Principle

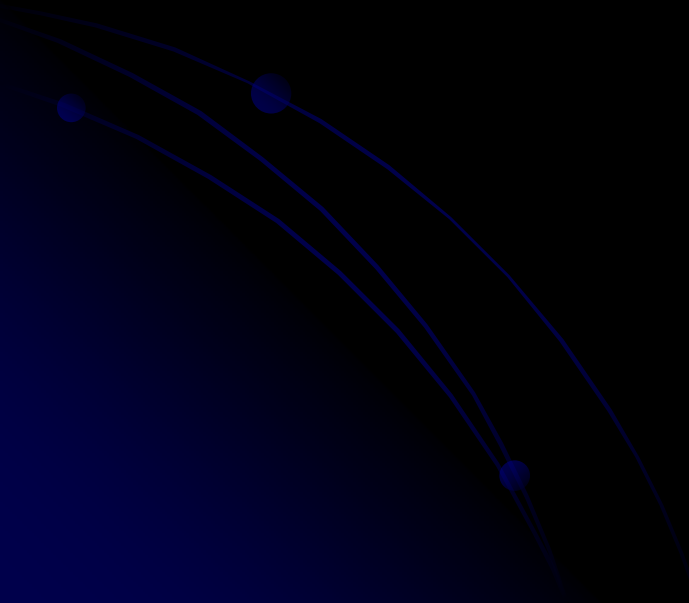

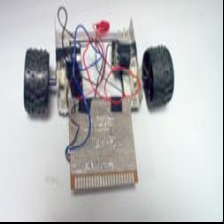

Single Sensor

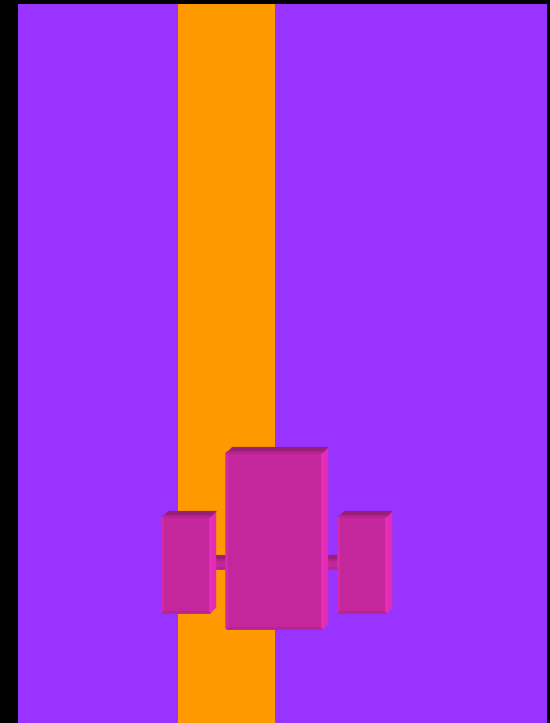
- ❁ Detects edge.
- ❁ Directs Power alternately to two motors.
- ❁ Advantages
 - Single sensor.
 - Suitable for sharp curves.
- ❁ Disadvantages
 - Jerky motion.
 - If robot leaves path
 - Turns 180' and moves in opposite direction






Dual Sensor

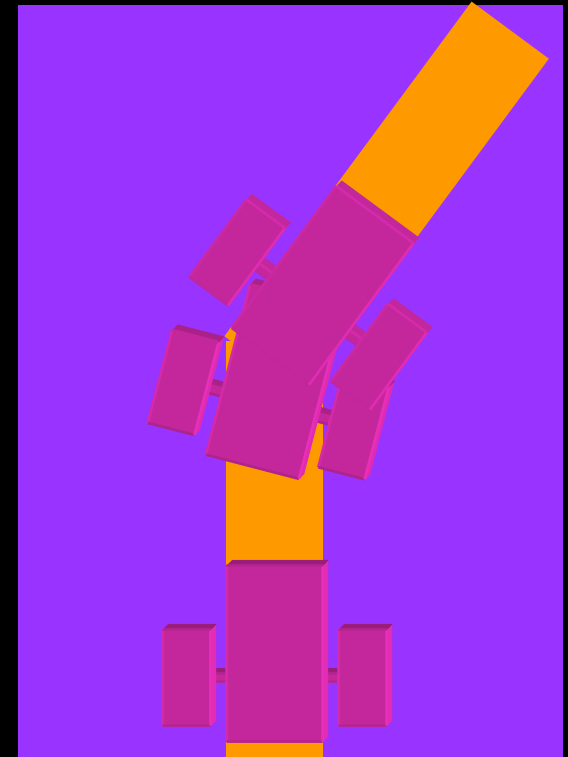- **Two LDR's.**
- **Each sensor controls one motor.**
 - **Left sensor controls right motor and vice versa**
- **Advantages**
 - **Smooth motion on straight line**
- **Disadvantages**
 - **Two Sensors**
 - **Two motors should be synchronized**




Components

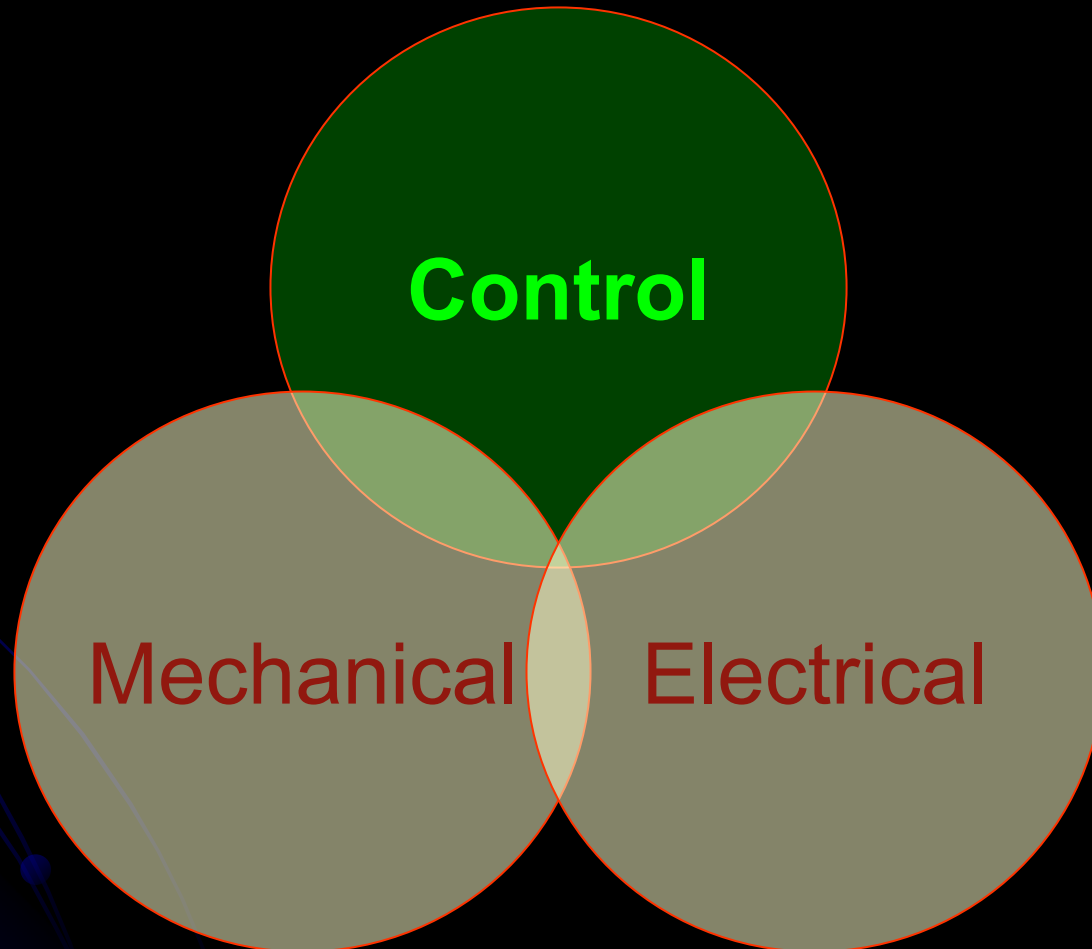

Light Dependent Resistor

Light dependent resistors

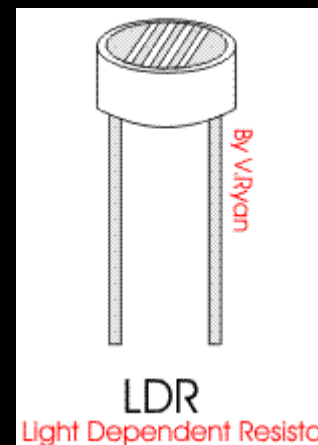- Electronic components where the resistance of the device varies with light intensity.
- Also called LDRs, photoresistors or photoconductors.
- Used to detect Presence of Light.
- Normally the resistance of an LDR is very high(1 M Ω).
- When illuminated with light resistance drops dramatically.




Light Dependent Resistor


Working

- Made of a high resistance semiconductor.
- Photons are absorbed by the semiconductor.
 - Bound electrons jump into the conduction band.
 - The resulting free electron (and its hole partner) conduct electricity, thereby lowering resistance.

Types

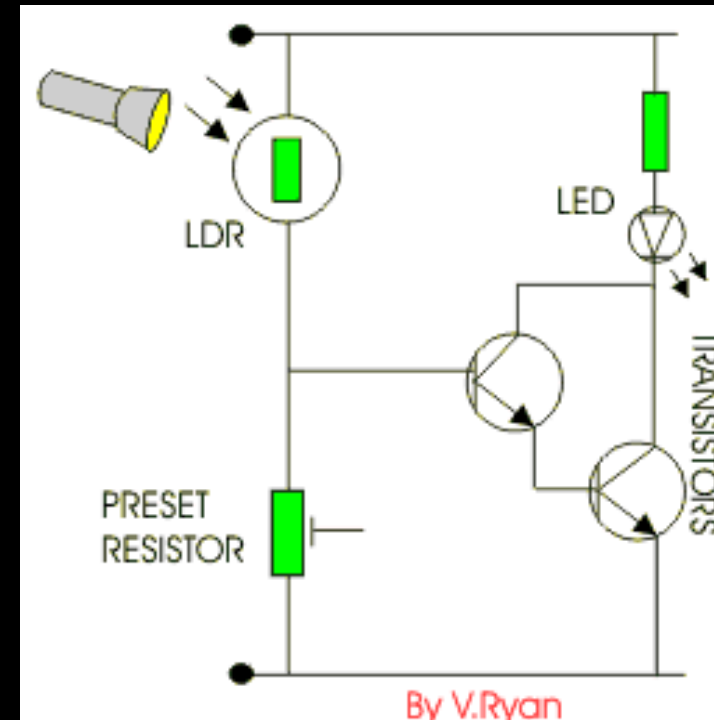
- **Cadmium sulfide (CdS) LDRs**
 - Camera light meters, clock radios, security alarms and street lights.
- **Ge:Cu photoconductors**
 - Far-infrared detectors.
 - Used for infrared astronomy and infrared spectroscopy.




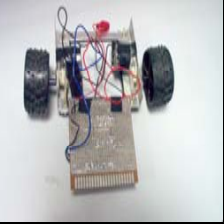


Light Emitting Diode

- Usually made of Aluminum-Gallium-Arsenide (AlGaAs).
- Pure aluminum-gallium-arsenide.
 - All of the atoms bond perfectly to their neighbors.
 - No free electrons to conduct electric current.
- In doped material.
 - Additional atoms change the balance, either adding free electrons or creating holes where electrons can go.
 - Makes the material more conductive.
- The interaction between electrons and holes generates light.

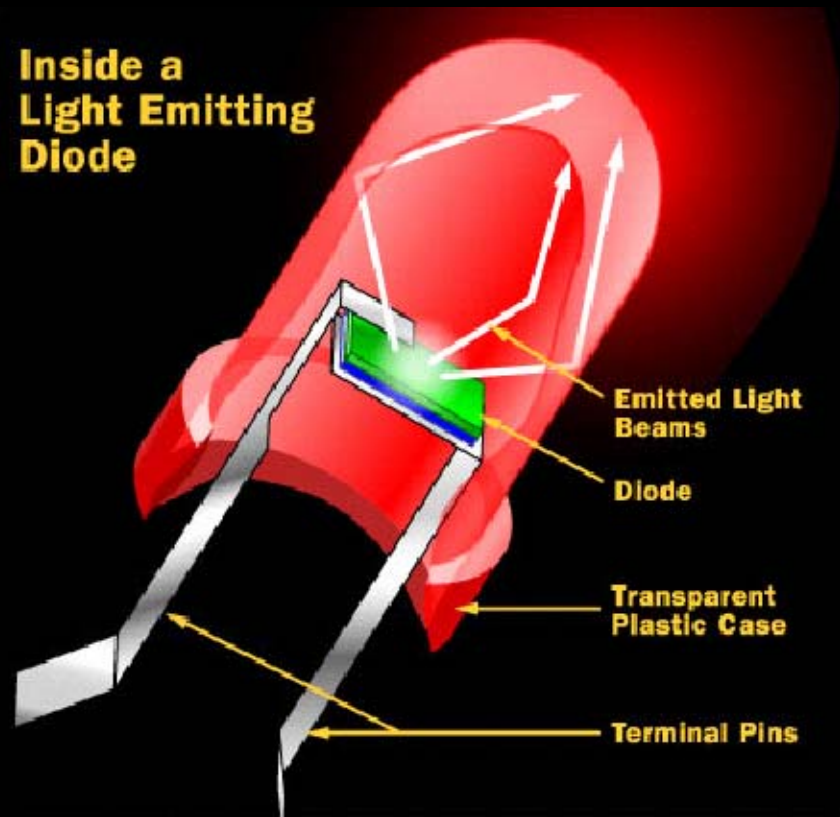

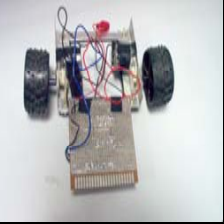


Working

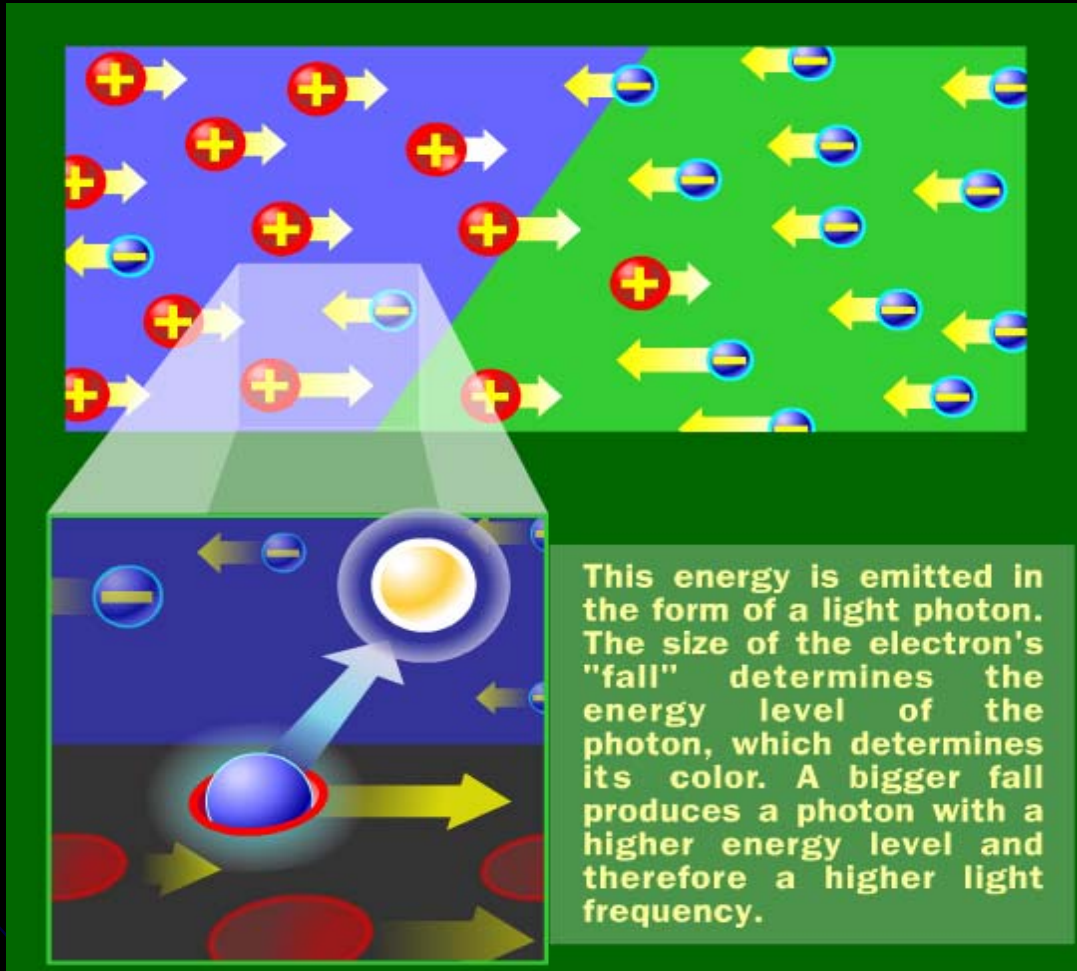

Voltage Comparator

- Compares two voltage signals and determines which one is greater.
- The result is indicated by the output voltage.
 - If the output is saturated in the positive direction.
 - Noninverting input (+) is a greater than the inverting input (-).
 - If the output voltage is near the negative supply voltage.
 - Inverting input (-) has a greater voltage applied to it than the noninverting input (+).
 - All voltages measured with respect to ground.




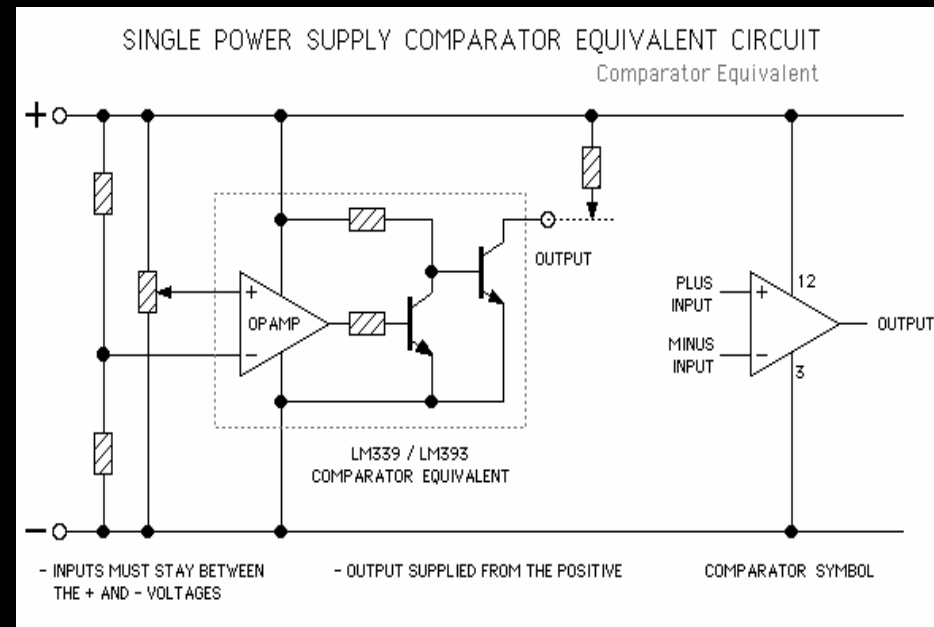


Operation

- Reference voltage
 - One-half of the supply voltage
- Input voltage
 - Variable from zero to the supply voltage.

BASIC OPERATION OF VOLTAGE COMPARATORS

Comparator Operation

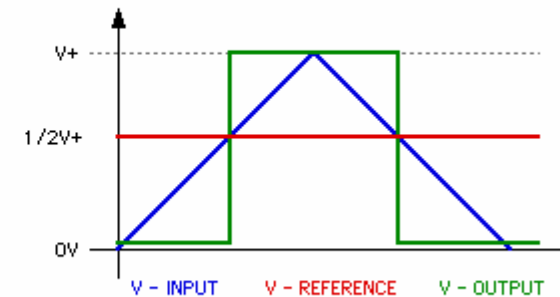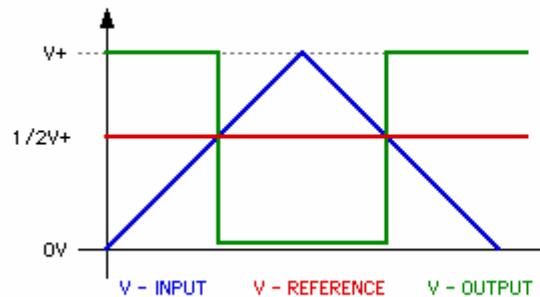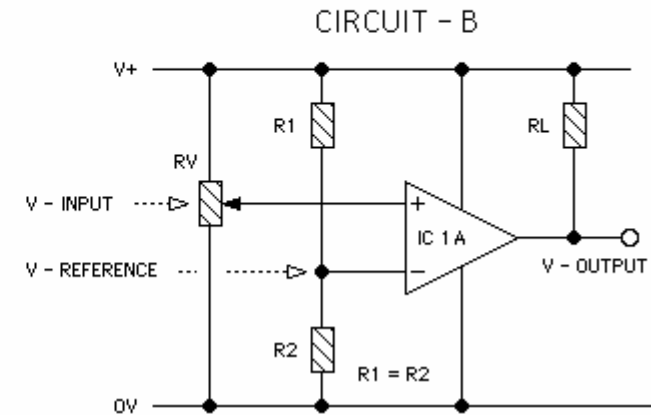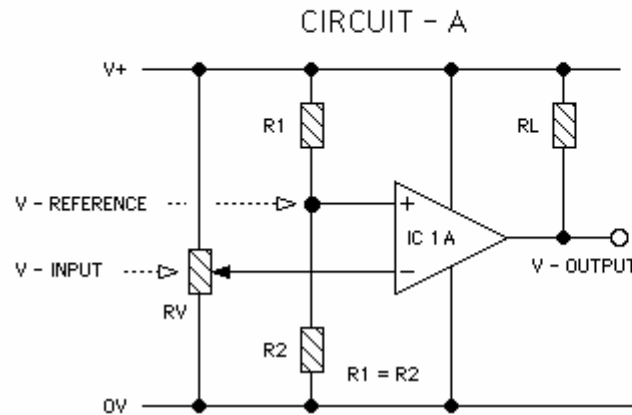

Actual and Ideal Comparator

❁ Voltage comparators are not perfect devices.


❁ Input Offset Voltage.

❁ This problem occurs when the Input voltage changes very slowly.

❁ Result of the Input Offset Voltage

❁ Output transistor does not fully turn on or off when the input voltage is close to the reference voltage.

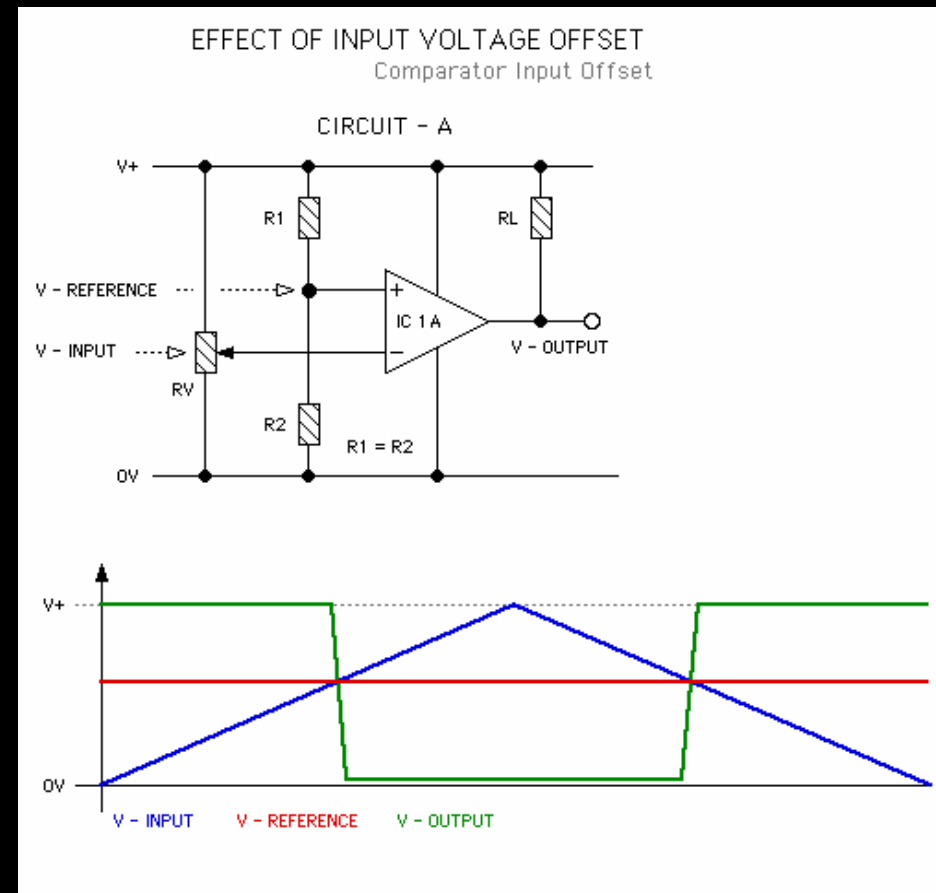❁ Keeping the value of R_L high will help reduce the problem.



LM339 Comparator IC



Features.



- High gain.
- Wide Bandwidth.


Application

- Limit comparators.
- Simple analog to Digital converters.
- Pulse, square wave and time delay generators.
- Clock timers.
- Multivibrators.
- High voltage digital logic gates.

Advantages

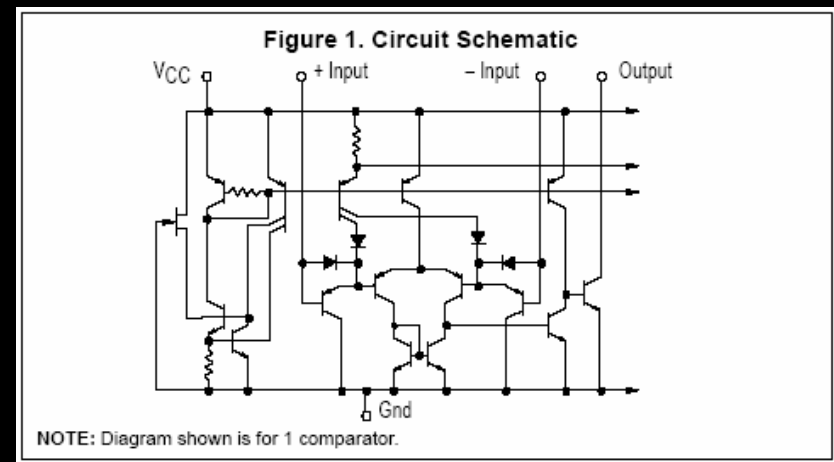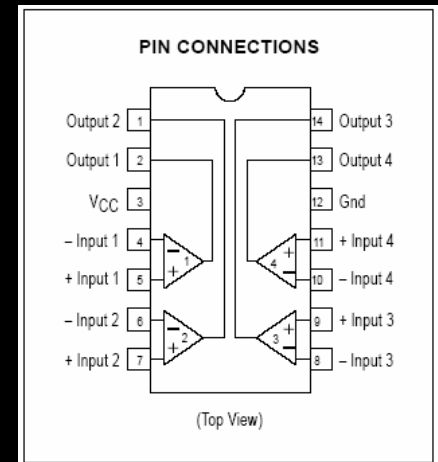- High precision comparators.
- Reduced V_{OS} drift over temperature.
- Eliminates need for dual supplies.
- Allows sensing near GND.
- Compatible with all forms of logic.
- Power drain suitable for battery operation.



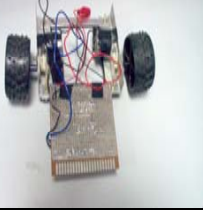


Transistor Switch

Switch open.


- No base current flows.
- No collector current can flow.
- The transistor is said to be CUT OFF.

Switch closed.

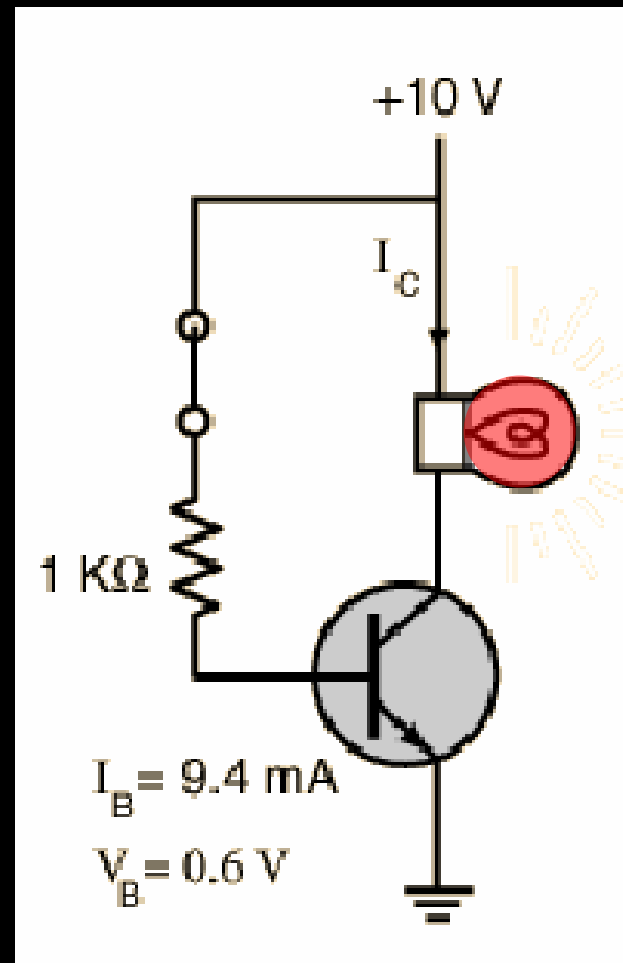
- Base current flows causing collector current to flow.
- The battery voltage is dropped across the lamp causing the collector voltage to fall to a very low value.
- The transistor is said to be SATURATED.




Components

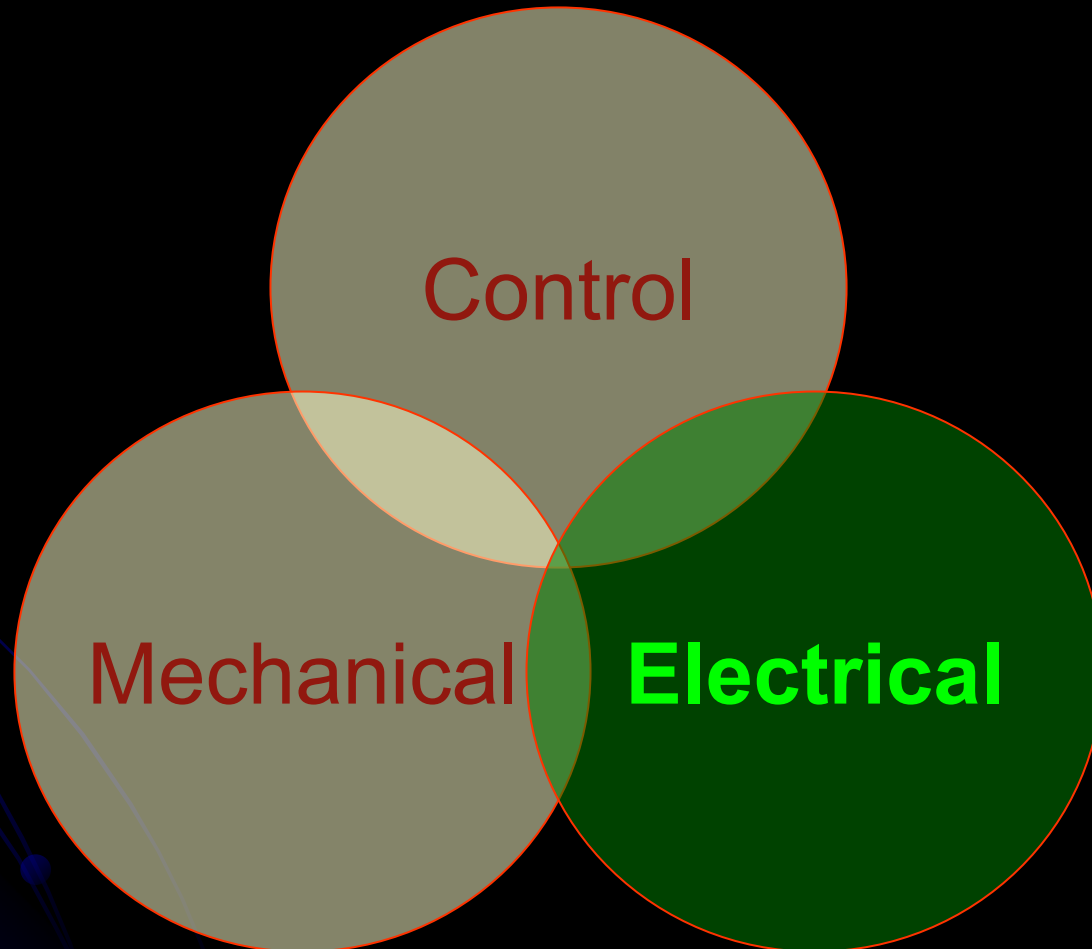


DC Motor

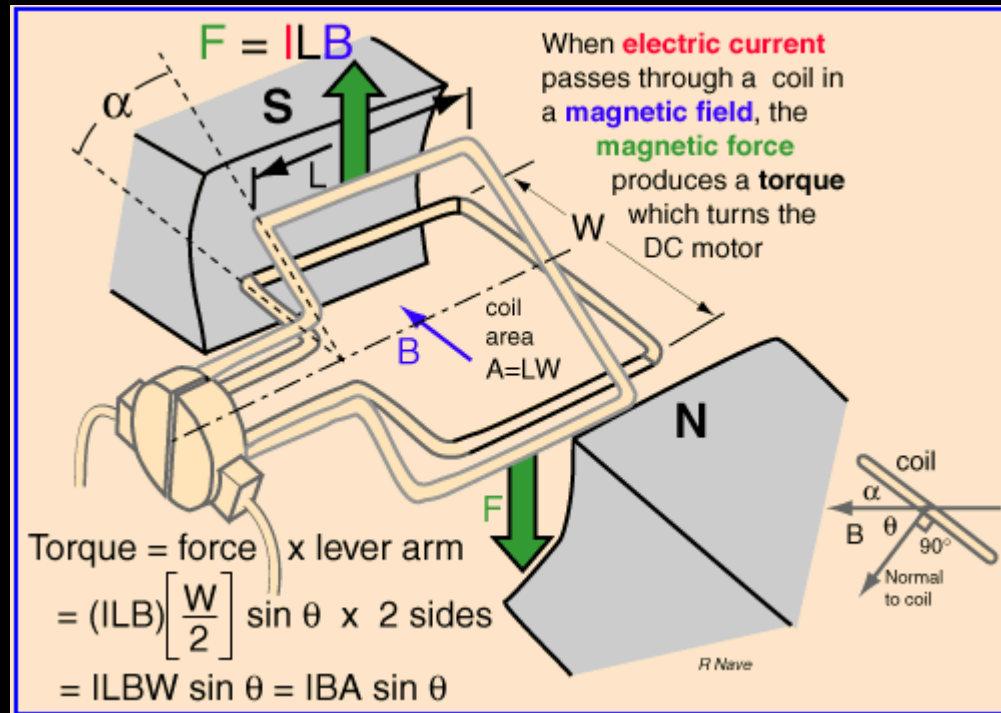


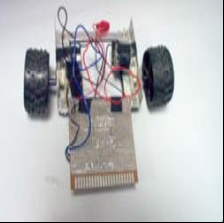


Complete Circuit

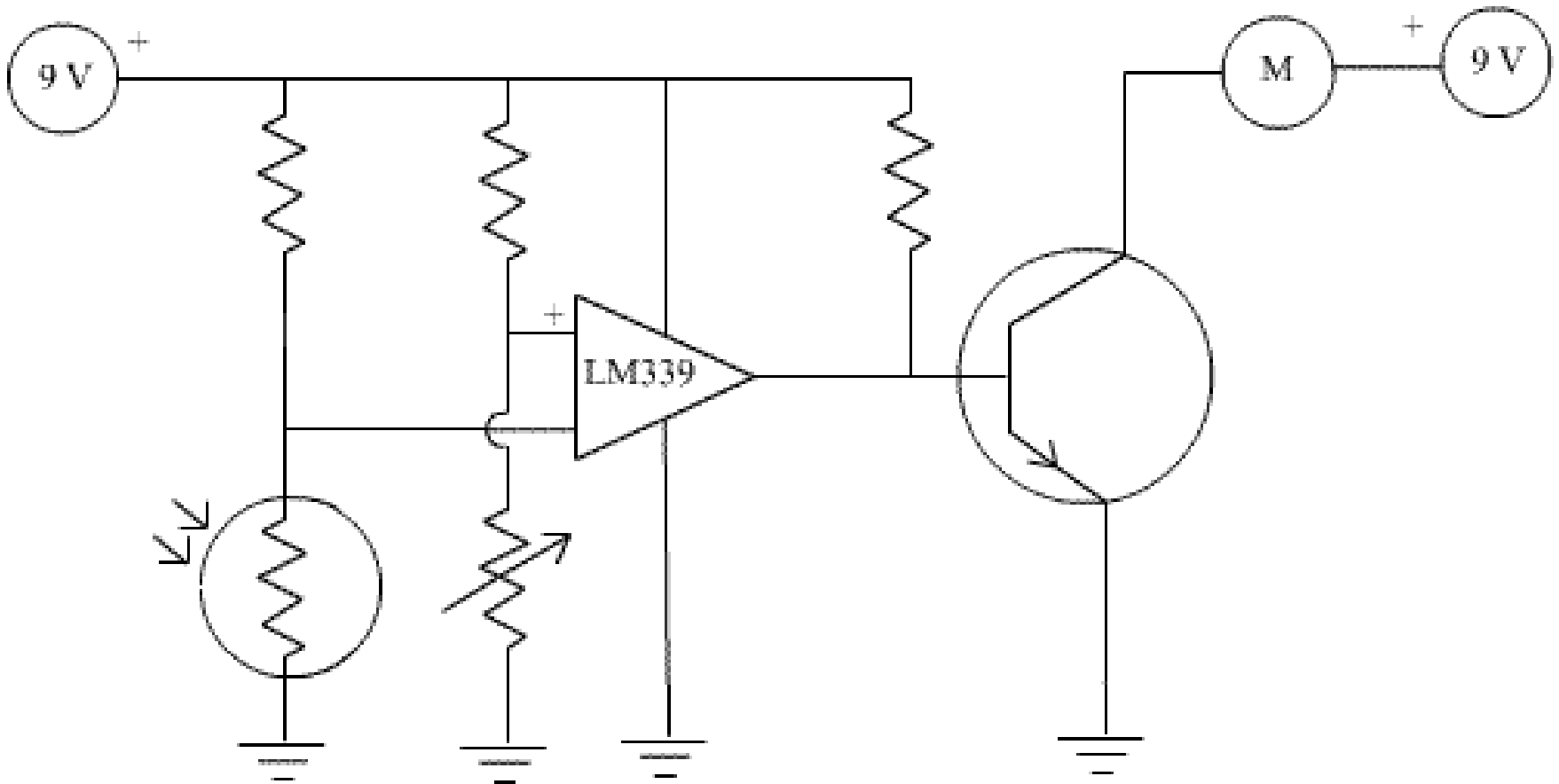



Components

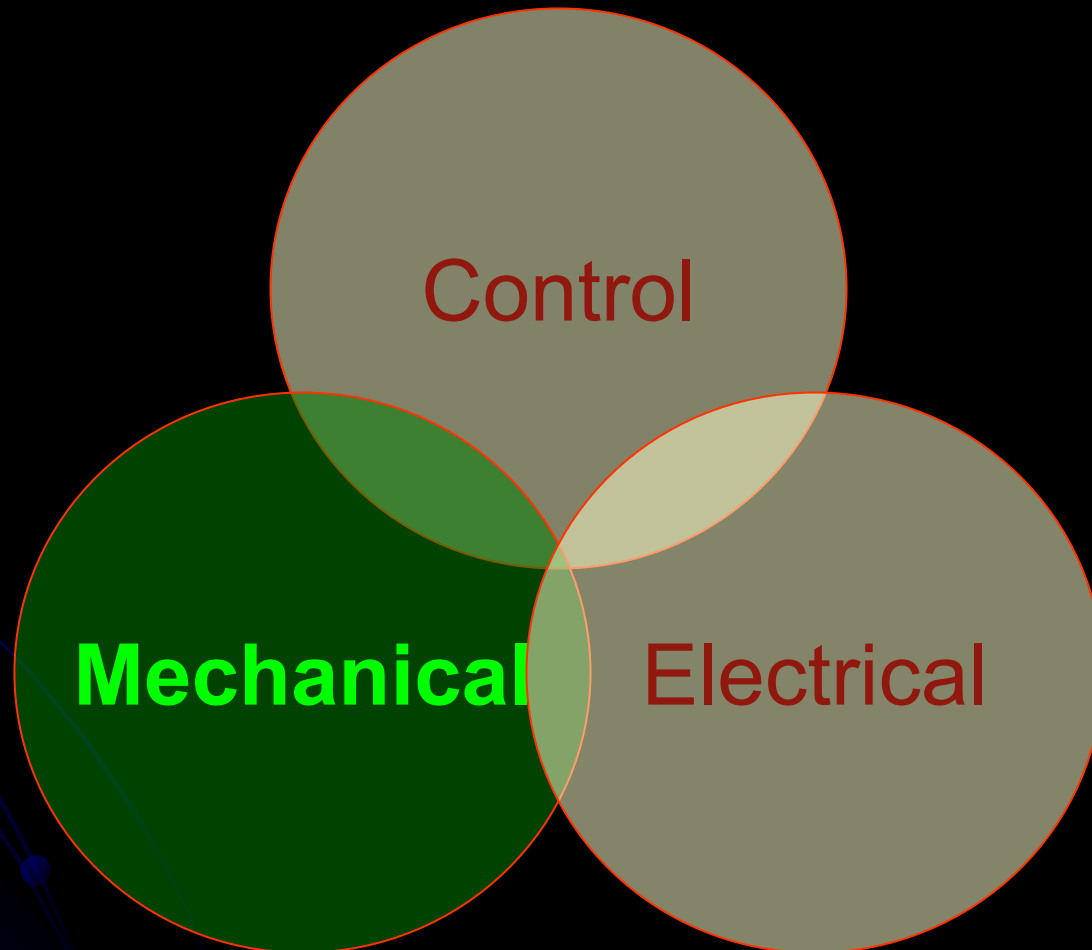

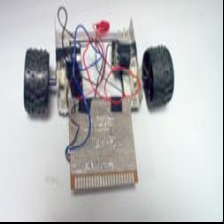


Gear Assembly

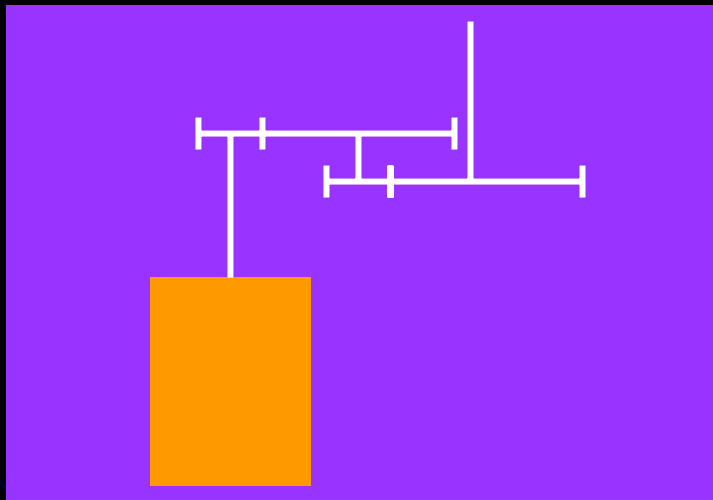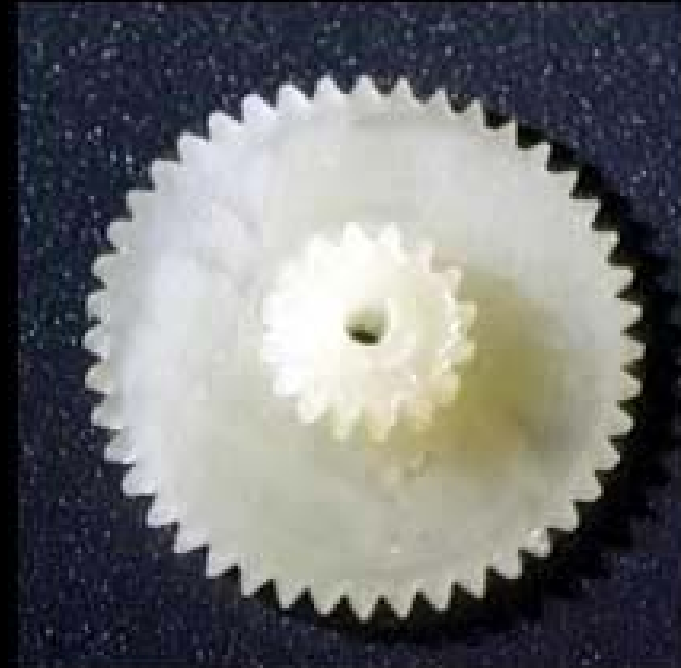- To improve the torque.
- Speed of DC Motor gets reduced.
- Ideal for Locomotion.
- 1:36 Gear reduction used.



Practical Problems

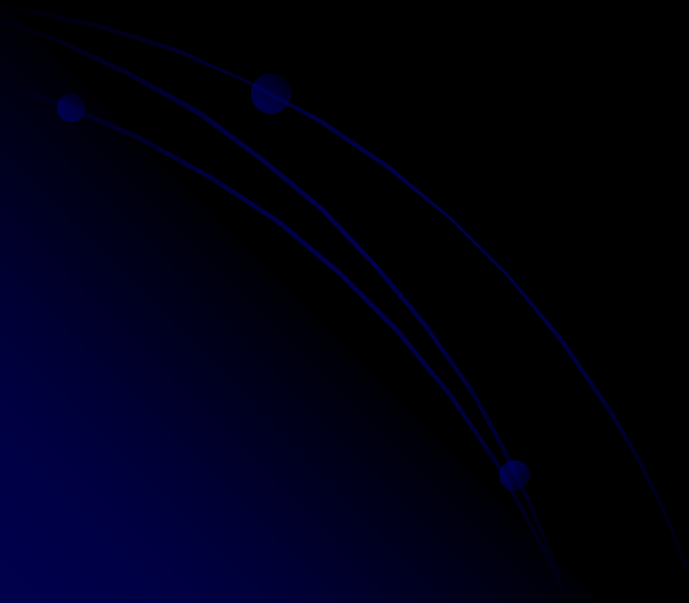



Electronic Problems

✿ LDR


- LDR Initially used had very high resistance (in $M\Omega$).
- New LDR's were not exactly the same.
 - One was 3 $K\Omega$, Other was 10 $K\Omega$.
 - Had to tune each circuit differently.

✿ LED

- The two LED's had different light intensity.
- Separating the two LED's

✿ Transistor

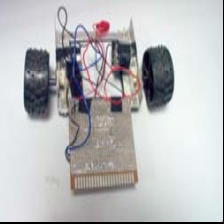- Initially BC107 used
 - Amperage rating was not high enough.
 - Gave rise to heating problems.
 - Replaced it with BDX530 which has a Heat sink.



Mechanical Problems

❁ Gear Assembly

- ❁ Was not very rigid.

❁ Direction of Motion


- ❁ Power not enough to push robot.
- ❁ Changed Motor position to pull the Robot.


❁ Friction

- ❁ High due to lack of third wheel.
- ❁ Teflon Tape helped to reduce friction.

❁ Height of Sensor.

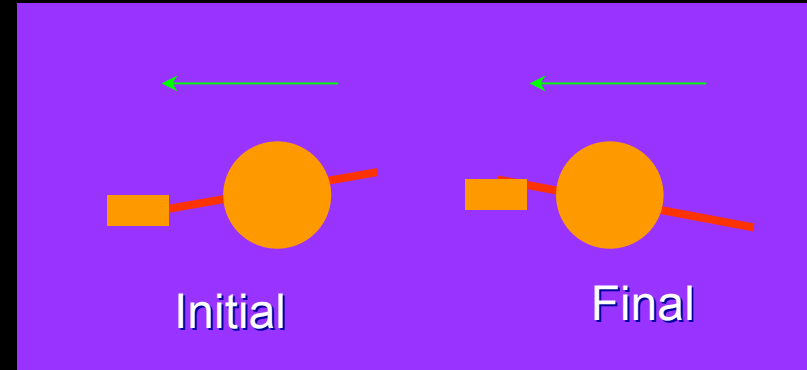
- ❁ Circuit to be calibrated based on height of Sensor from the ground.



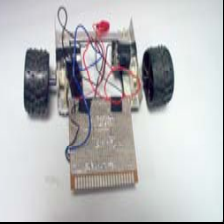

Possible Improvements

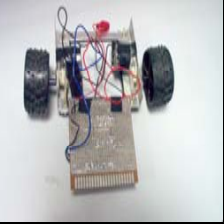- ✿ **Have separate power source for Control circuit and Motor.**
- ✿ **Improve mechanical drive train.**
- ✿ **Include**
 - ✿ **Microprocessor.**
 - ✿ **Collision and obstacle avoidance.**
 - ✿ **Multiple AGV.**



References

- ✿ **Robot Room.**
 - ✿ **Line following Robots**
- ✿ **How Stuff Works Website.**
- ✿ **Sarjoun Skaffet. et.al, Inertial Navigation and Visual Line Following for a Dynamic Hexapod Robot.IEEE, 2003.**